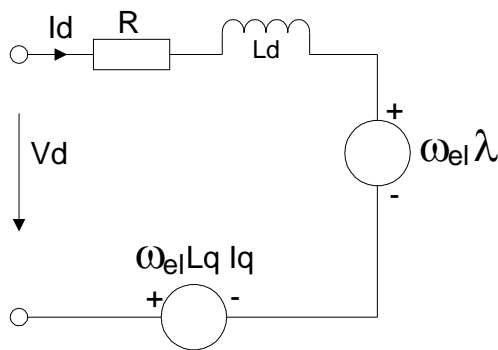





Determination of synchronous inductances L_d and L_q of IPMSM and PMSM

The equivalent phase model of PMSM and IPMSM are shown below (PSPM = permanent magnet synchronous motors). R represents the sum of ohmic losses (R_{ohm}) plus magnetic losses (R_m). L_d and L_q are the equivalent inductances along the d-axis (direct axis) and the q-axis (quadrature axis).



d-axis circuit

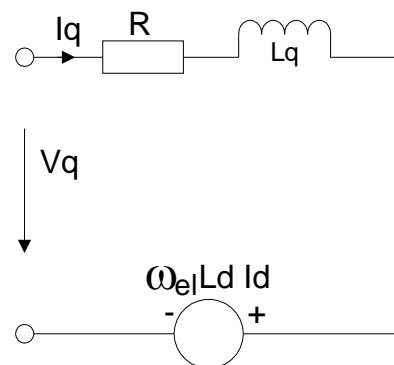


q-axis circuit

The ohmic losses are temperature dependent $R_{ohm} = R_o(1+\alpha\Delta t)$, the magnetic losses are magnetization dependent due to non-linearity.

L_d and L_q are measured in a locked motor shaft test. This implies $\omega_{el} = 0$, or the voltage sources of the equivalent circuits are zero.

L_q , and mainly L_d are somewhat current dependent.


Measure d-axis inductance L_d

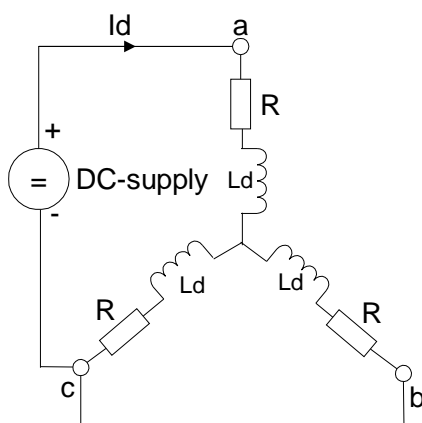

Alignment into d-axis

- Step 1: Align the rotor to phase a. Connect DC-supply as shown. The current I_d aligns the rotor into the d-axis, electrical angle = 0° .
- Step 2: Lock the rotor shaft.
- Step 3: Replace the DC-supply by a variable frequency AC-Source. Apply current I_d .
- Step 4: From the 108A display read frequency f , $|Z_{01}|$, Φ_{01} , (use current synchronization).
- Step 5: Calculate: $R = 0.667 \cdot |Z_{01}| \cos(\Phi_{01})$
 $X_d = 0.667 \cdot |Z_{01}| \sin(\Phi_{01})$
 $L_d = X_d / 2\pi f$
- Step 6: Repeat Step 5 at different current levels. Plot R and L_d versus current.


Measure q-axis inductance L_q

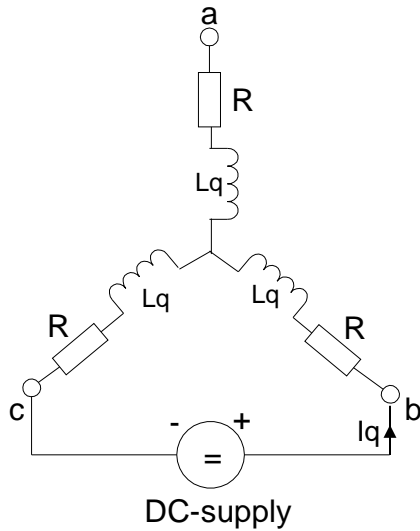

Alignment into q-axis

- Step 1: Current I_q aligns the rotor into the q-axis, electrical angle = 90° .
- Step 2: Lock the rotor shaft firmly, I_q generates torque.
- Step 3: Replace the DC-Supply by a variable frequency AC-Source. Apply current I_q .
- Step 4: From the 108A display read frequency, $|Z_{01}|$, Φ_{01} , (use current synchronization).
- Step 5: Calculate: $R = 0.5 |Z_{01}| \cos(\Phi_{01})$
 $X_q = 0.5 |Z_{01}| \sin(\Phi_{01})$
 $L_q = X_q / 2\pi f$
- Step 6: Repeat step 5 at different current levels. Plot L_q versus current.

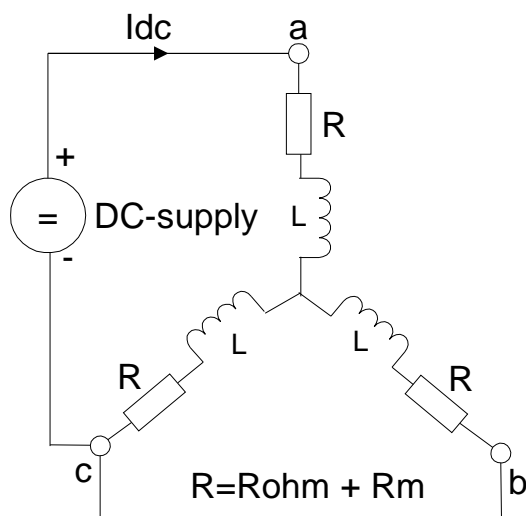Measure Ohmic component of Loss resistance $R = R_{ohm} + R_m$




- Step 1: Connect DC power supply.
- Step 2: Measure V_{dc} , I_{dc} , and P_{dc} using 108A.
- Step 3: Calculate $R_{ohm} = P_{dc} / I_{dc}^2$



Back – EMF (BEMF)

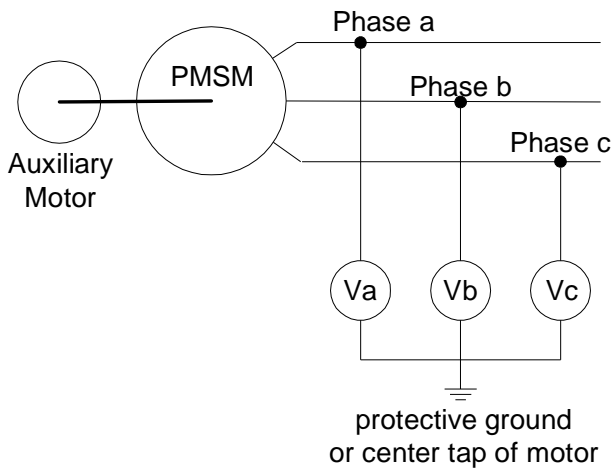To measure the BEMF the shaft of a PMSM / IPMSM is turned by an auxiliary motor at constant speed ω_{el} .



Step 1: Connect Va, Vb, Vc to phase 1, 2, 3 of the 108A. (use voltage synchronization).

Step 2: Display V01a, V01b, V01c the fundamental of voltage and frequency.

Step 3: Calculate the BEMF peak value.

$$V_{peak} = 1.41 \cdot V01a$$

$$V_{bpeak} = 1.41 \cdot V01b$$

$$V_{cpeak} = 1.41 \cdot V01c$$

Calculate $k = V_{peak} / 2\pi f$ [Vs / rad].

k is a constant used for motor control.